



University of Regina
Faculty of Engineering
MidTerm ENEL 384
Digital Logic November 13, 1998

One 8x11 crib sheet allowed(original)
Questions are 20% each


R.J.Palmer

1. Design a MOD 12 asynchronous counter using JK flip-flops.

Jeremiah Worby

2. The waveforms below are applied to a negative edge triggered JK flip-flop initially in the RESET state. Determine the timing waveform for Q.


Zara

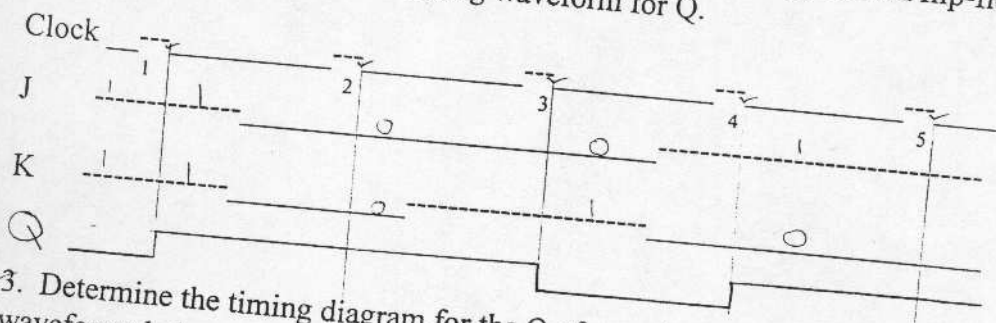

20

3. Determine the timing diagram for the Q of a positive edge triggered D flip-flop, using the timing waveforms below:

Tam Bui

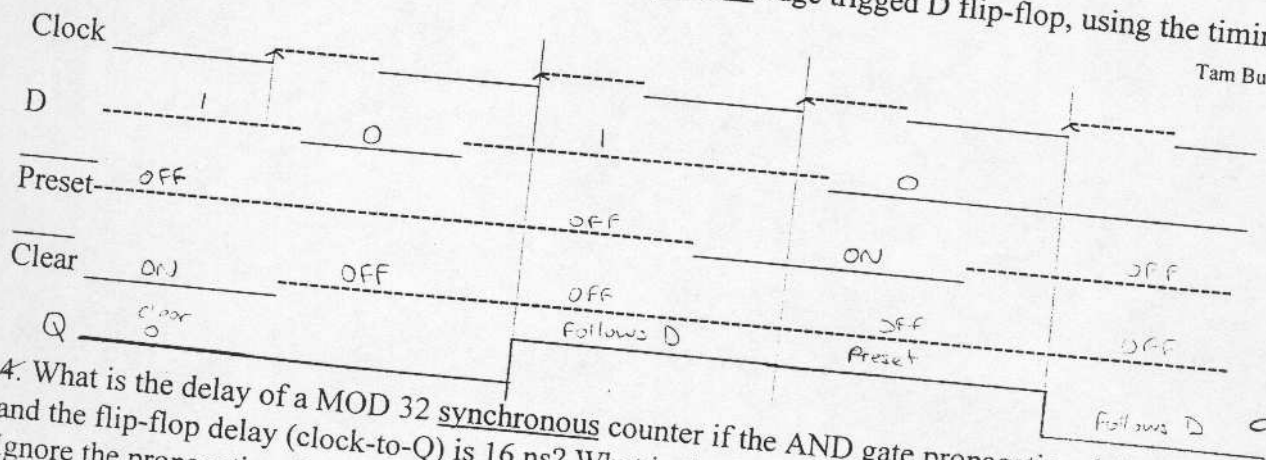

20

4. What is the delay of a MOD 32 synchronous counter if the AND gate propagation delay is 8 ns and the flip-flop delay (clock-to-Q) is 16 ns? What is the maximum clocking rate? Ignore the propagation delay of the routing.

Chad Delmuller

5. Design a divide-by-40 using D flip-flops. Make the design synchronous.

Dave Nguyen

1. MOD 12 async. counter J-K FFs.

1000

1001

1010

1011

1100 ← 12


1101 ← 13

decode next state

1101

4 3 2 1

4 flip flops

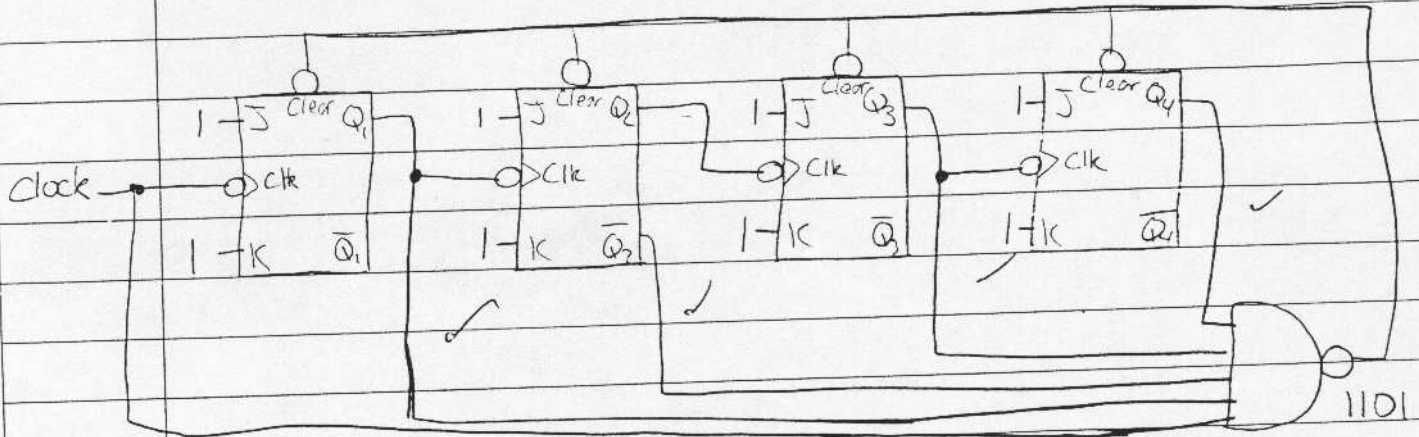

-connect clock to NAND to prevent glitching

20